

# Computer Architecture Lec 5a

Dr. Esti Stein

(Partly taken from Dr. Alon Schclar slides)

Based on slides by:

**Prof. Myung-Eui Lee**

Korea University of Technology & Education  
Department of Information & Communication

Taken from: **M.**

**Mano/Computer Design and  
Architecture 3<sup>rd</sup> Ed.**

# An Instruction

- A group of bits that instructs the computer to perform a specific operation.
- An instruction is usually divided into parts.




A group of bits that defines an operation:  
add, subtract, shift, and etc.

An address in the memory


$n$  bits define  $2^n$  operations

# A Stored Program Organization

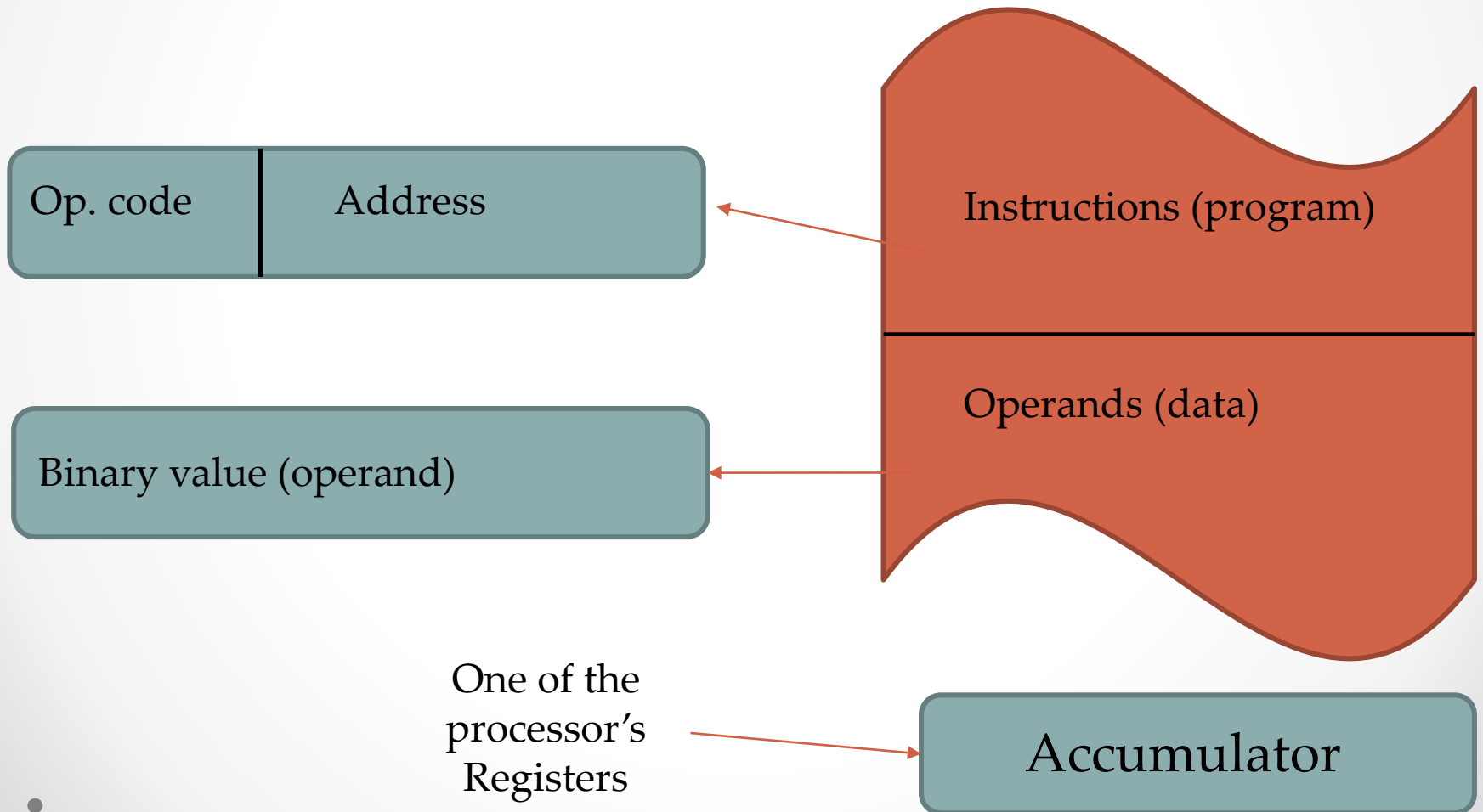
 
# The Instruction

All instructions and operands are 16 bits



**Size of memory is  $4096 \times 16$**

If an operation in the instruction does not need a memory operand, the rest of the bits can be used to expand the operation.

Examples:

clear accumulator, complement accumulator, read a character from the keyboard, etc.

# Addressing Modes

Op. code	Value or opcode extension
----------	---------------------------

**Immediate addressing mode**

0	Op. code	address in memory
---	----------	-------------------

**Direct addressing mode**


Indirect bit

3 bits remains  $\Rightarrow$  8 possible operations


1	Op. code	address of address in memory (pointer)
---	----------	--

**Indirect addressing mode**


# Addressing Modes

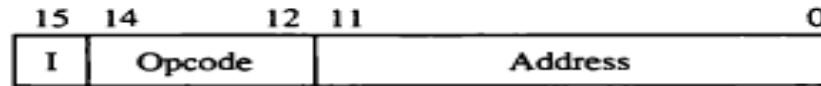

(a) Instruction format

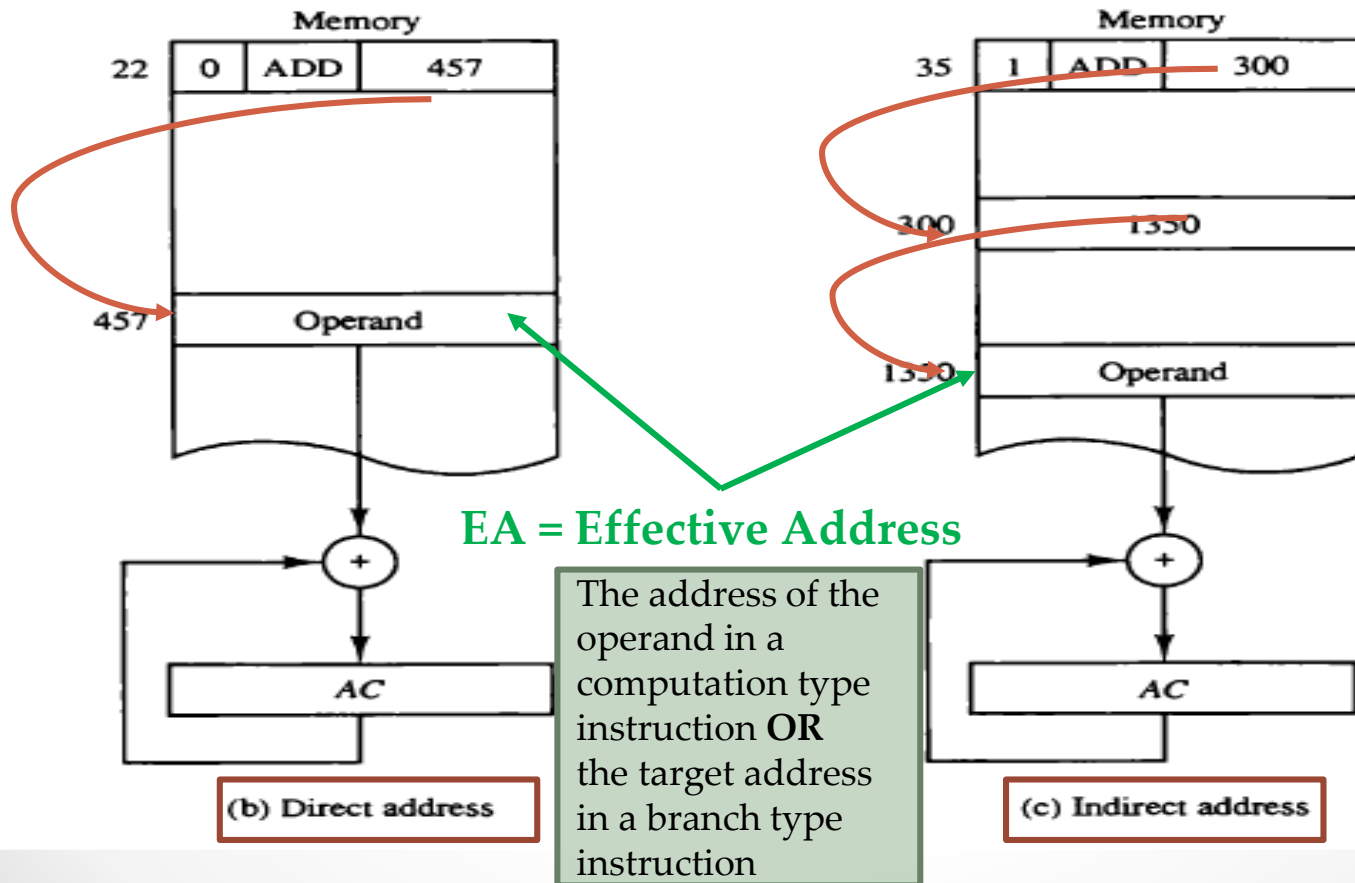

# Computer Registers

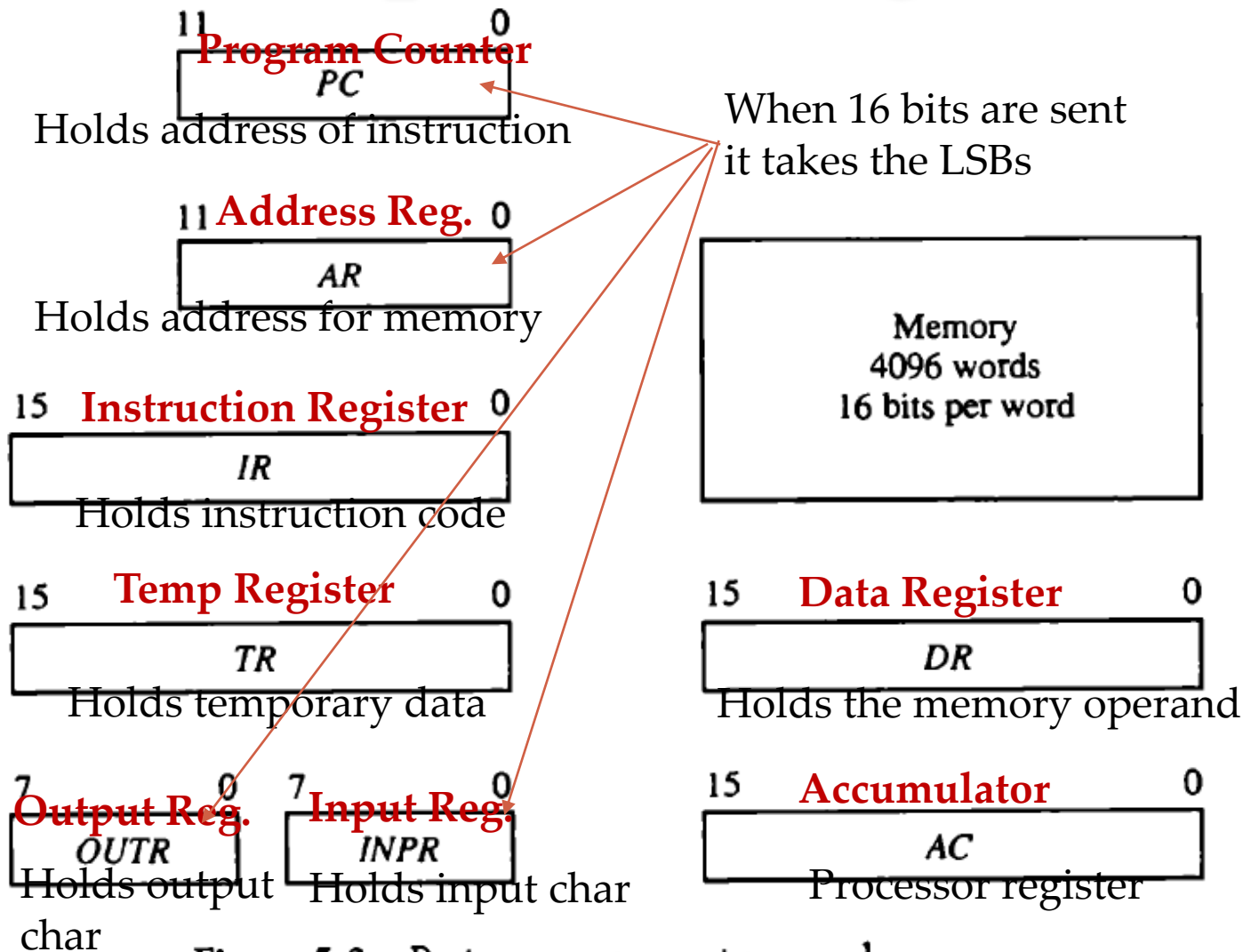

**Figure 5-3** Basic computer registers and memory.

# Register with INC, LD, CLR

AC  
AR  
DR  
PC  
TR

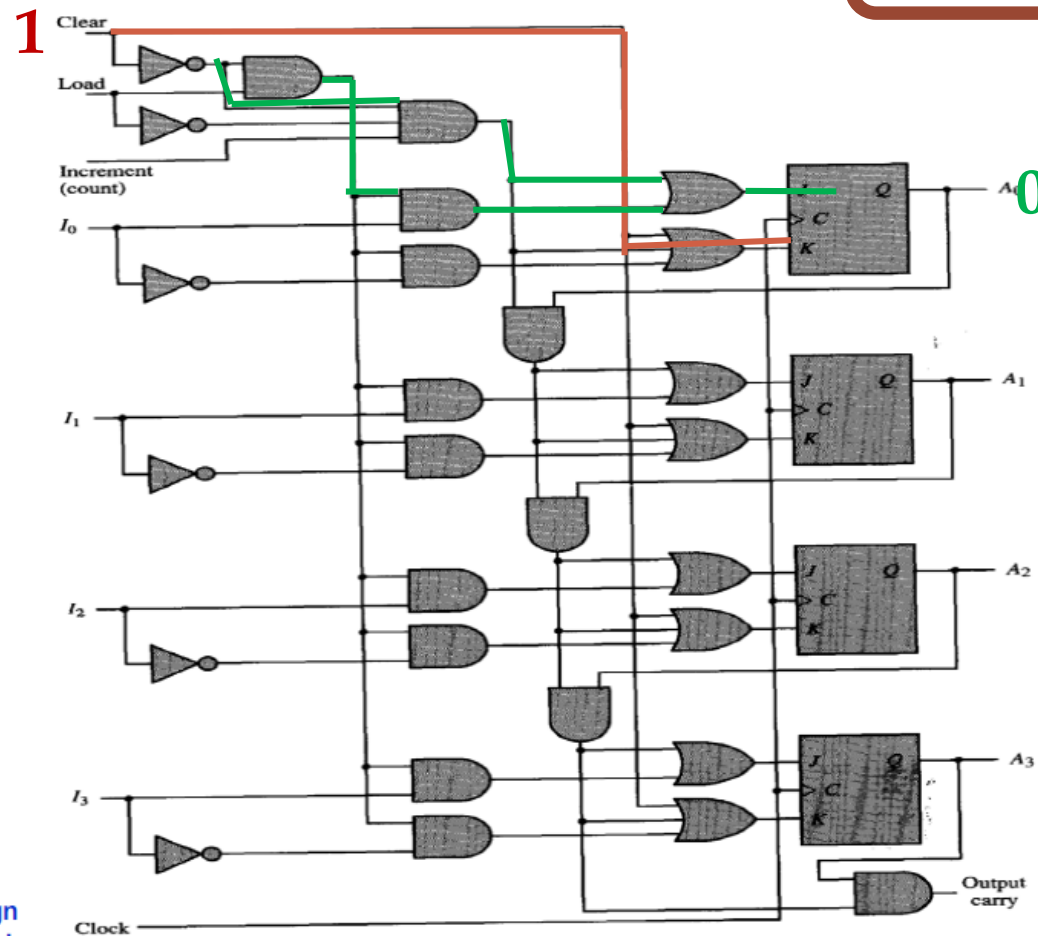



Figure 2-11 4-bit binary counter with parallel load and synchronous clear.

Taken from: M.  
Mano/Computer Design  
and Architecture 3<sup>rd</sup> Ed.



# Register with INC, LD, CLR

AC  
AR  
DR  
PC  
TR

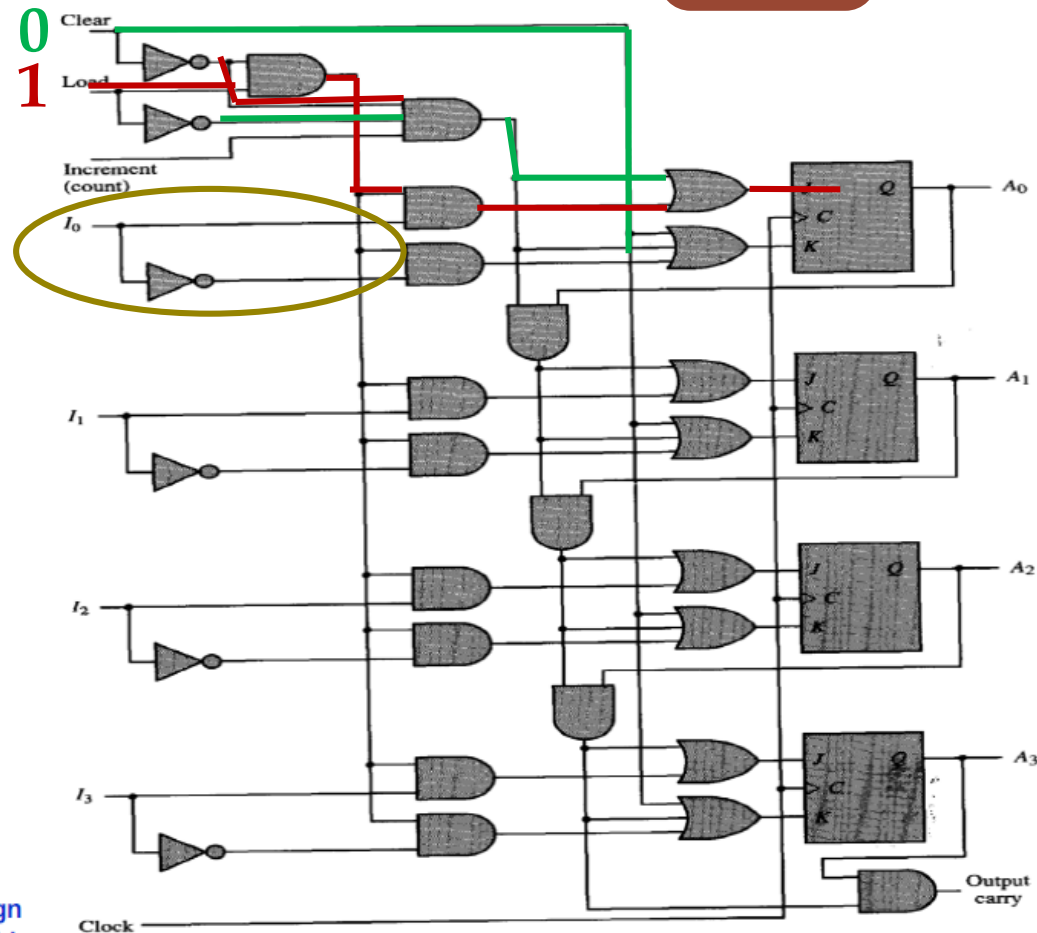

Taken from: M.  
Mano/Computer Design  
and Architecture 3<sup>rd</sup> Ed.

Figure 2-11 4-bit binary counter with parallel load and synchronous clear.

# Register with INC, LD, CLR

AC  
AR  
DR  
PC  
TR

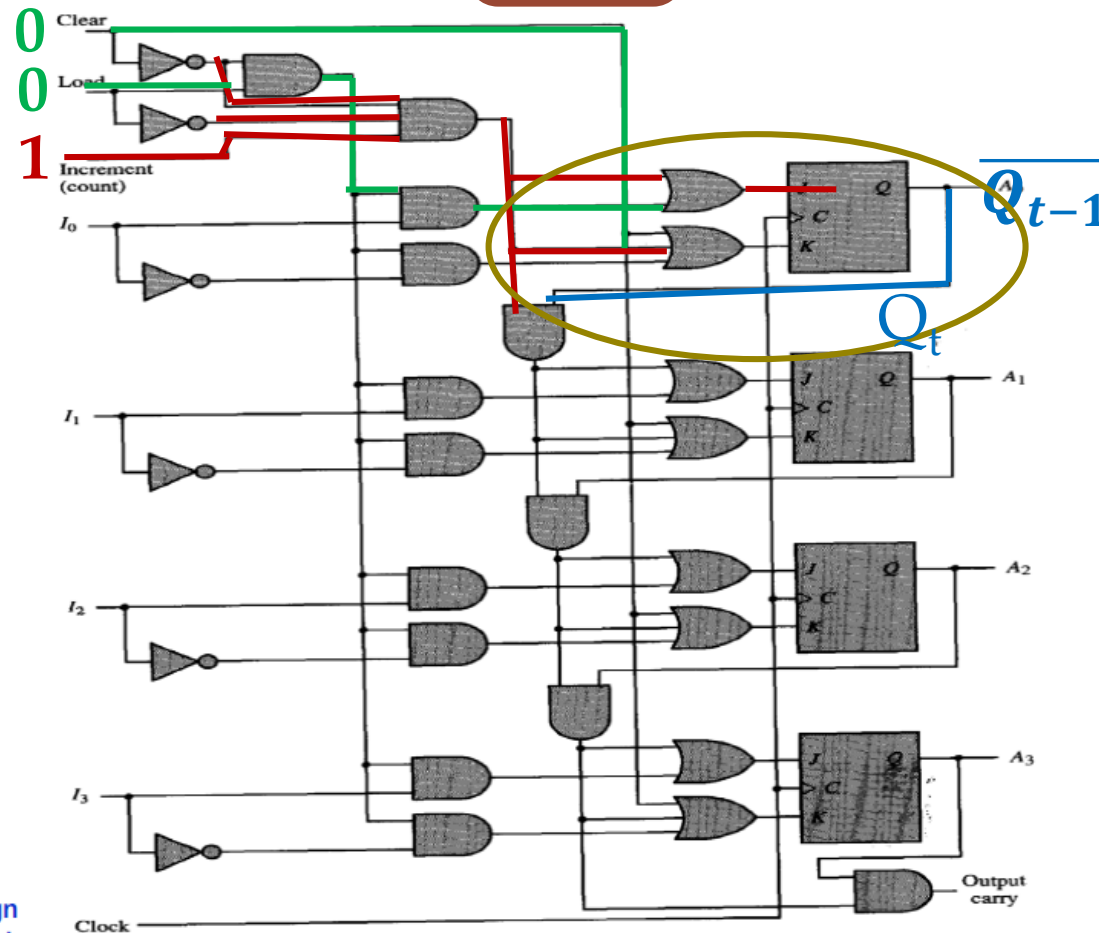


Figure 2-11 4-bit binary counter with parallel load and synchronous clear.

Taken from: M.  
Mano/Computer Design  
and Architecture 3<sup>rd</sup> Ed.

# The Bus

## The bus

Perform A&L ops  
On AC and DR

CONTROL  
UNIT

No direct bus path  
from mem to AC

Taken from: M.  
Mano/Computer Design  
and Architecture 3<sup>rd</sup> Ed.

Choose which register will go into the bus


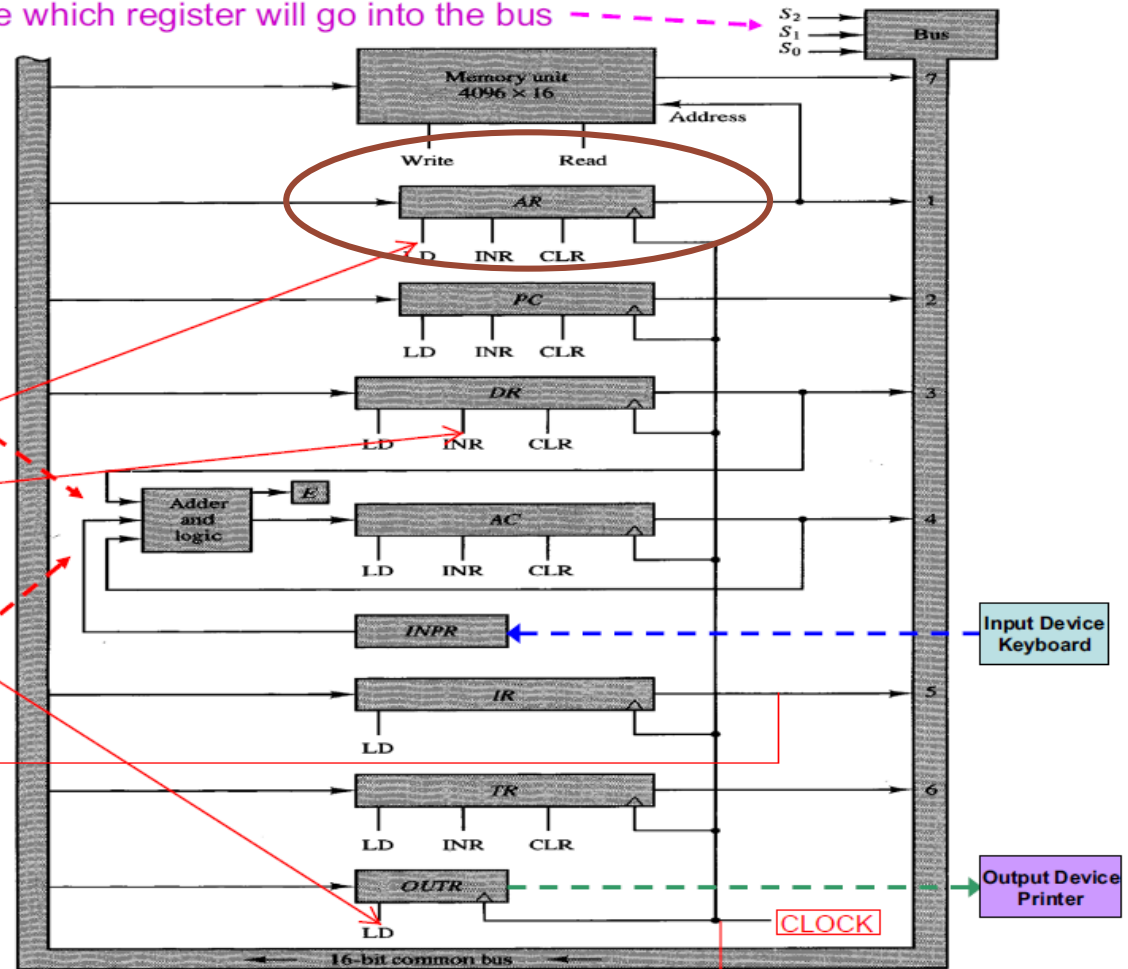


Figure 5-4 Basic computer registers connected to a common bus.

Alon Schclar, Tel-Aviv College, 2009

# Reminder – register with parallel load

IR  
OUTR

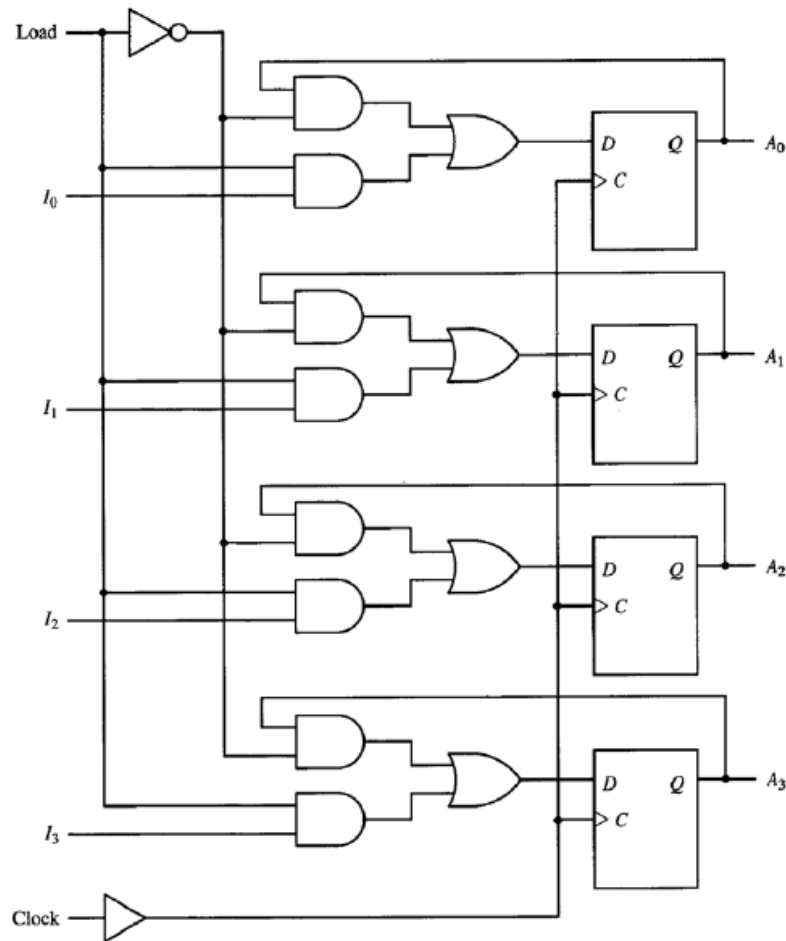


Taken from: M.  
Mano/Computer Design  
and Architecture 3<sup>rd</sup> Ed.

Figure 2-7 4-bit register with parallel load.

Alon Schclar, Tel-Aviv College, 2009

# The clock cycle

 

# The Bus

» Accumulator(**AC**) : 3 Path

- 1) Register Microoperation : clear AC, shift AC,...
- 2) Data Register : add DR to AC, and DR to AC  
End carry bit set/reset), memory READ

$D_2T_4 : DR \leftarrow M[AR]$

$D_2T_5 : AC \leftarrow DR, SC \leftarrow 0$

- 3) INPR : Device  
Adder & Logic

» **Note**) Two microoperations can be executed at the same time

$DR \leftarrow AC : s_2s_1s_0 = 100(4), DR(\text{load})$

$AC \leftarrow DR : DR \rightarrow \text{Adder \& Logic} \rightarrow AC(\text{load})$

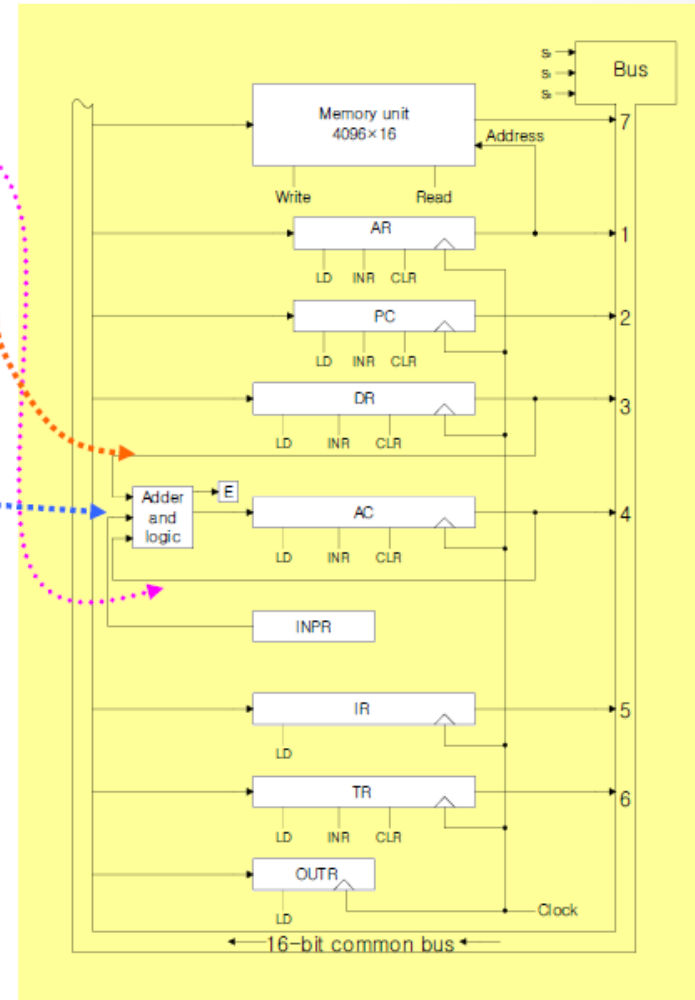


Fig. 5-4 Basic computer registers connected to a common bus


# The Bus - examples

## • $TR \leftarrow DR$

- Place DR on BUS
  - $S_2S_1S_0=011$  (DR num is 3)
- Insert BUS content to TR
  - Enable LD (load) input of TR

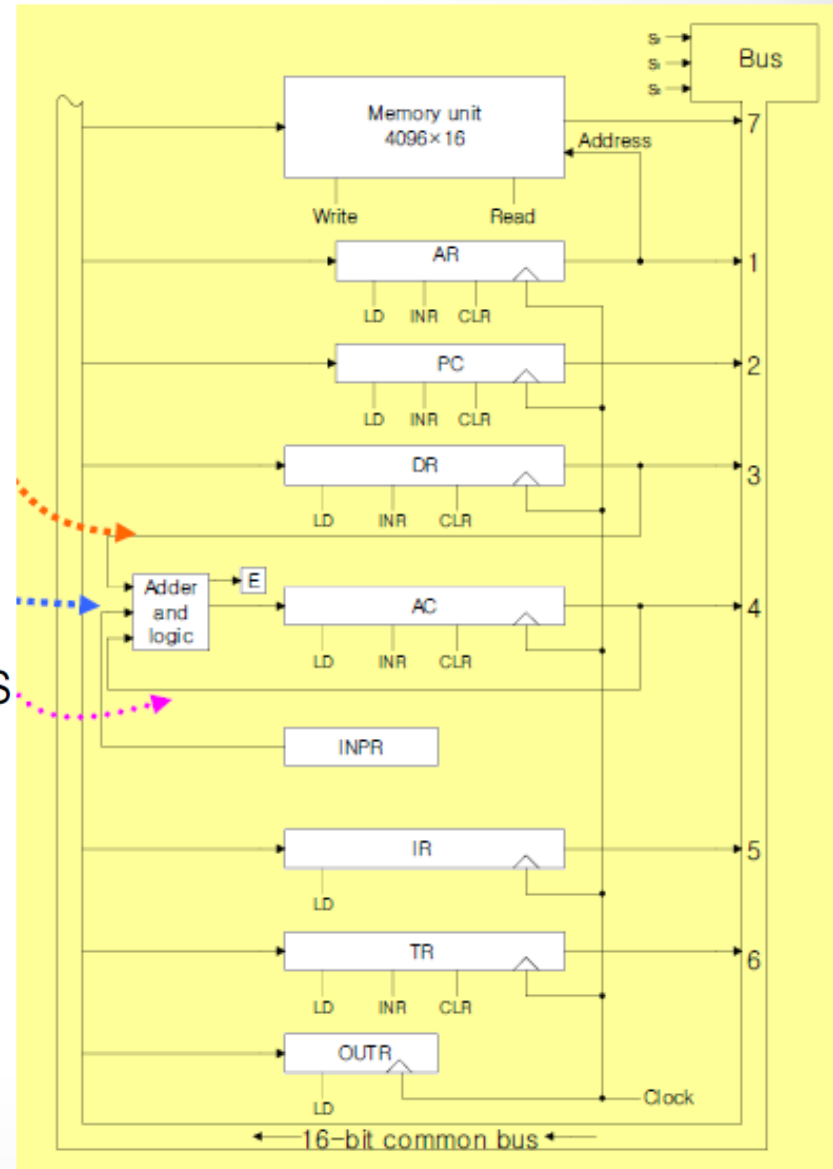
## • $DR \leftarrow MEM[AR]$

- AR is connected to address input of MEM
- Enable READ input of MEMORY
- Place MEMORY content (MEM[AR]) on BUS
  - $S_2S_1S_0=111$  (MEM num is 7)
- Insert BUS content to DR
  - Enable LD (load) input of DR


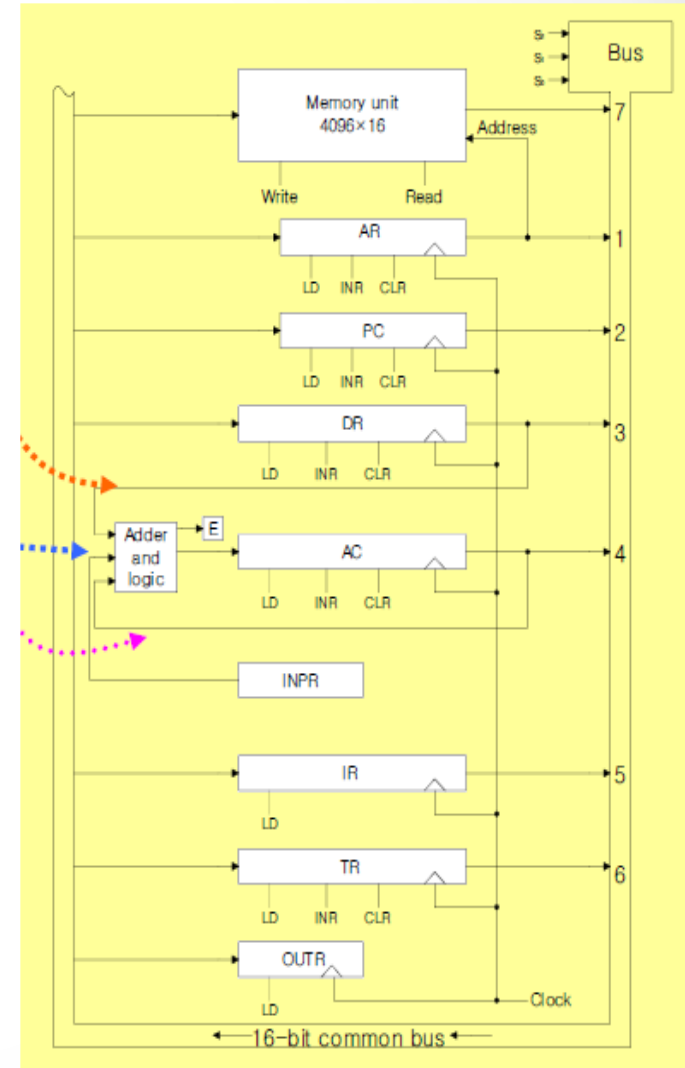
# The Bus – concurrent data transfer

- During the same clock cycle
  - The content of any register can be applied onto the bus and
  - an operation can be performed in the adder and logic circuit
- The clock transition at the end of the cycle
  - transfers the content of the bus into the target register and
  - the output of the adder and logic circuit into AC.





# The Bus – concurrent data transfer


- **DR ← AC**

- Place AC on BUS
  - $S_2S_1S_0=100$  (AC num is 4)
- Insert BUS content to DR
  - Enable LD (load) input of DR

- **AC ← DR**

- DR connected to AC via the **Adder & Logic** (aka A&L or ALU)
- Instruct ALU to let DR pass through
- Enable LD (load) input of AC

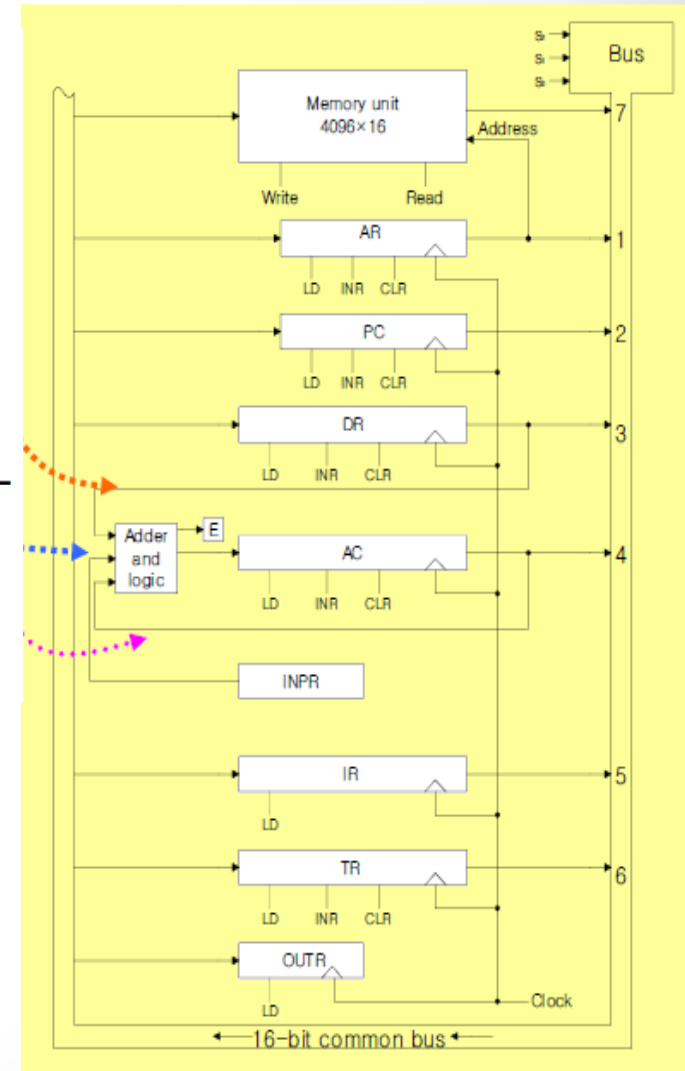- **Can be executed in the same clock cycle**



# Computer Instruction

## ■ 5-3 Computer Instruction


### ◆ 3 Instruction Code Formats : *Fig. 5-5*

#### ● Memory-reference instruction

» Opcode = 000 ~ 110


■ I=0 : 0xxx ~ 6xxx, I=1: 8xxx ~ Exxx

I=0 : Direct,  
I=1 : Indirect

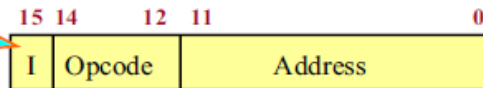


#### ● Register-reference instruction

» 7xxx (7800 ~ 7001) : CLA, CMA, ....

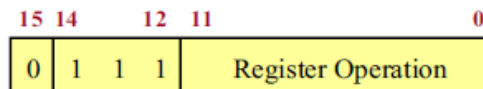
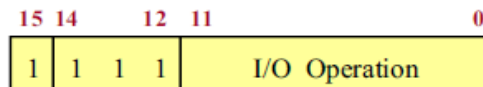
#### ● Input-Output instruction

» Fxxx(F800 ~ F040) : INP, OUT, ION, SKI, ....



Symbol	Hex Code		Description
	I = 0	I = 1	
AND	0xxx	8xxx	And memory word to AC
ADD	1xxx	9xxx	Add memory word to AC
LDA	2xxx	Axxx	Load memory word to AC
STA	3xxx	Bxxx	Store content of AC in memory
BUN	4xxx	Cxxx	Branch unconditionally
BSA	5xxx	Dxxx	Branch and Save return address
ISZ	6xxx	Exxx	Increment and skip if zero
CLA		7800	Clear AC
CLE		7400	Clear E
CMA		7200	Complement AC
CME		7100	Comp m e
CIR		7080	Circulate right AC and E
CIL		7040	Circulate left AC and E
INC		7020	Increment AC
SPA		7010	Skip next instruction if AC positive
SNA		7008	Skip next instruction if AC negative
SZA		7004	Skip next instruction if AC zero
SZE		7002	Skip next instruction if E is 0
HLT		7001	Halt computer
INP		F800	Input character to AC
OUT		F400	Output character from AC
SKI		F200	Skip on input flag
SKO		F100	Skip on output flag
ION		F080	Interrupt
IDF		F040	Inter

# Instruction Set Completeness

A computer should have a set of instructions so that the user can evaluate any function that is known to be computable.

A complete set must include sufficient number of instructions from the following categories:

1. Arithmetic, logical, and shift - **CMA, INC, CIR, AND..**
2. Moving information between the registers, and between the registers and memory – **LDA, STA**
3. Program control, and status check – **BUN, ISZ, BSA..**
4. Input and output – **INP, OUT..**

**A complete set of instructions, but not efficient.**

# Timing and Control

## ◆ Clock pulses

- A master clock generator controls the timing for all registers in the basic computer
- The clock pulses are applied to all F/Fs and registers in system
- The clock pulses do not change the state of a register unless the register is enabled by a control signal
- The control signals are generated in the control unit
  - » The control signals provide control inputs for the multiplexers in the common bus, control inputs in processor registers, and microoperations for the accumulator

# Two (major) Types of Control Organization

## Hardwired Control (This chapter)

- » The control logic is implemented with gates, F/Fs, decoders, and other digital circuits
- » + Fast operation, - Wiring change (if the design has to be modified)

## Microprogrammed Control (chapter 7)


- » The control information is stored in a control memory, and the control memory is programmed to initiate the required sequence of microoperations
- » + Any required change can be done by updating the microprogram in control memory, - Slow operation

# The Control Unit


The Sequence Counter (SC) is incremented synchronously:

$T_0, T_1, T_2, T_3, \dots$

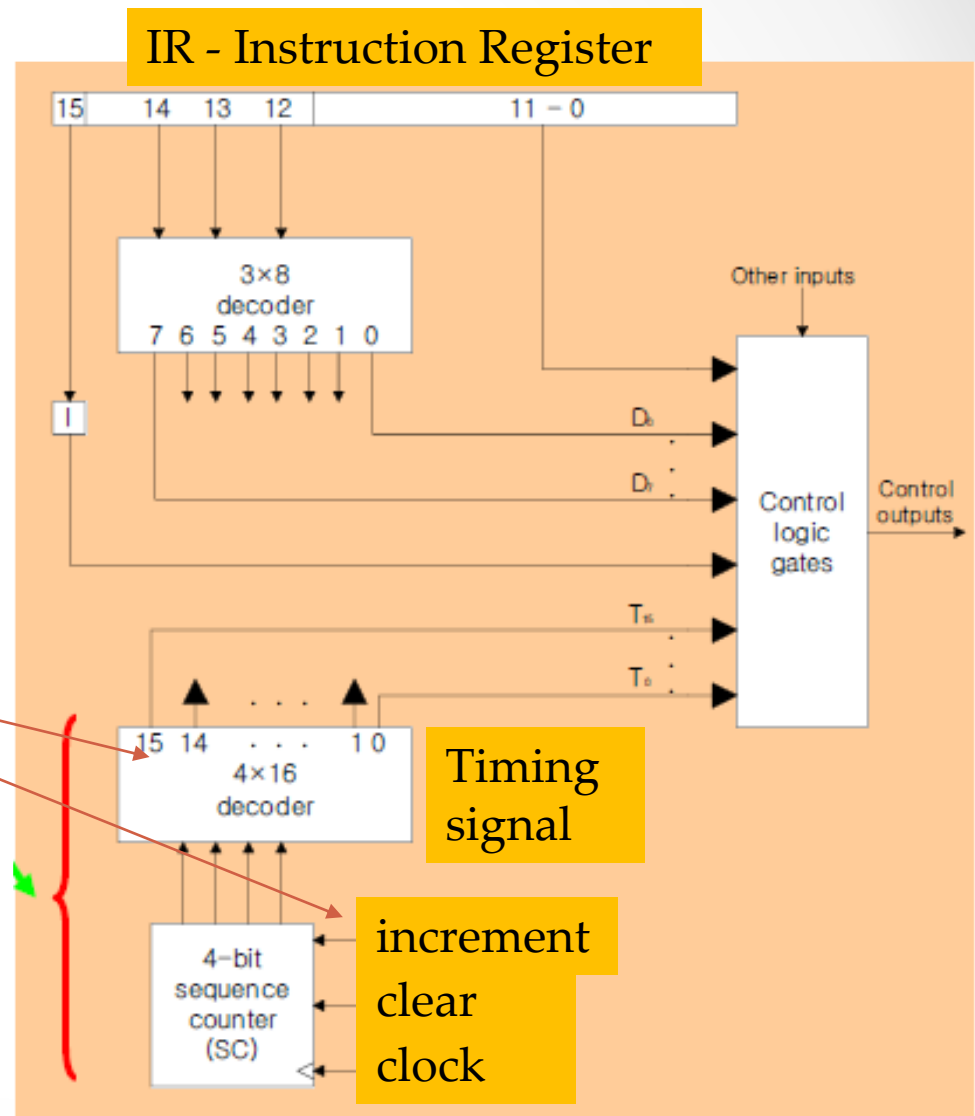The SC is cleared when in  
RTL we write  
symbolically:  
 $SC \leftarrow 0$



# The Control Unit

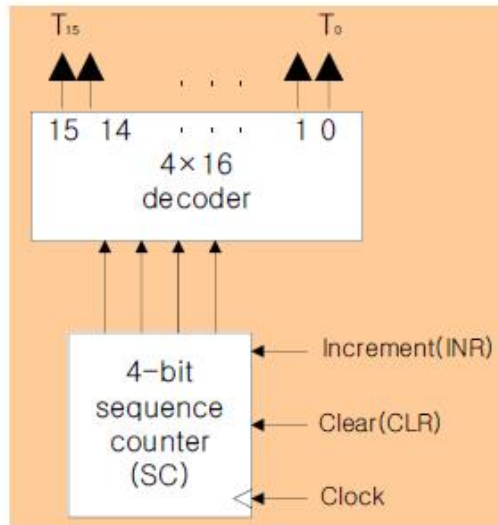

$D_3T_4 : SC \leftarrow 0$

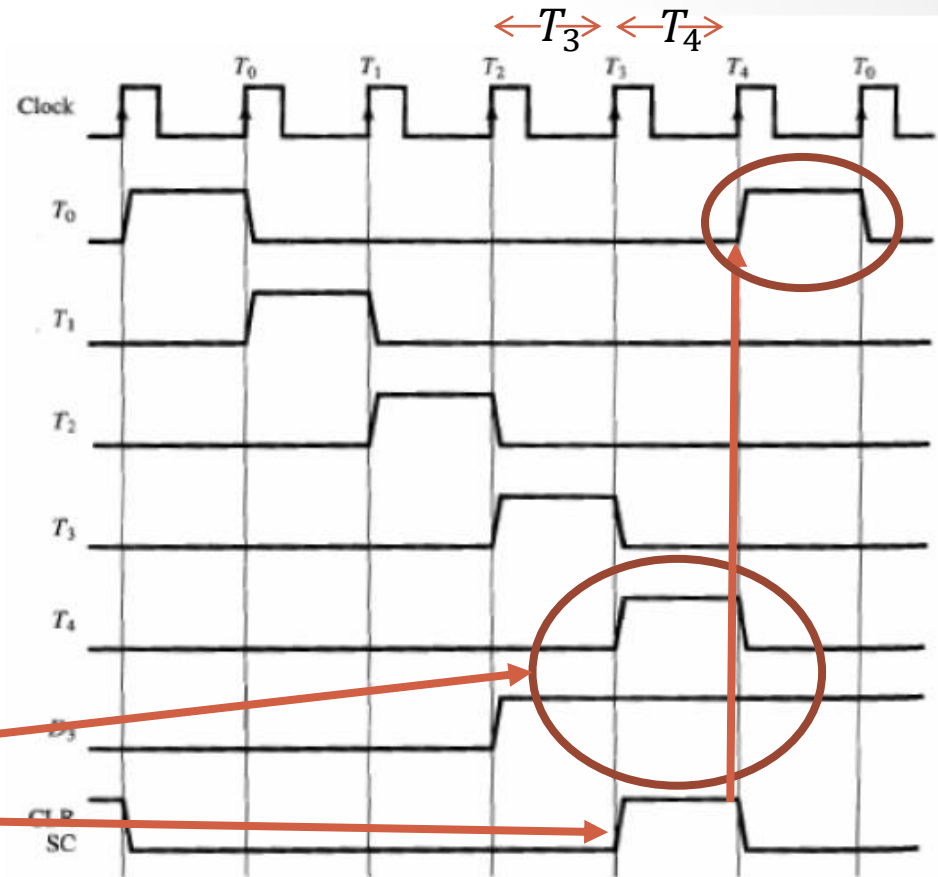


Figure 5-7 Example of control timing signals.

Taken from: M. Mano/Computer Design and Architecture 3<sup>rd</sup> Ed.



# Clock and Memory

- The memory read/write cycle is initiated with the rising edge of a timing signal.
- It is assumed that a memory cycle time is less than the clock cycle time.
- The memory R/W cycle is complete by the time the next clock goes through its positive cycle.
- This assumption is not valid in most of computers.



# Clock and Timing Signals

Example:

$$T_0 : AR \leftarrow PC$$

1.  $T_0$  is active during the entire clock cycle interval.
2. During this time the content of the PC is placed onto the bus, and the LD of AR is enabled.
3. The actual transfer occurs when the clock goes through a positive transition (end of cycle).
4. On positive transition SC goes from 0000 to 0001.
5.  $T_1$  is active and  $T_0$  is inactive.